

 


National Tsing Hua University, Taiwan  
EE-6250 超大型積體電路測試 (VLSI Testing)  
(Closed-Book) Midterm Exam., Fall Semester, 2023 (April 17, 2023)  
(七大題，總分 100 分)

 1. (10%) Answer the following questions.
  - (a) Consider three stuck-at faults,  $\{f_1, f_2, f_3\}$  for a circuit under test. Assume that  $f_1$  dominates  $f_2$  and  $f_2$  dominates  $f_3$ . By the transitive rule, we know  $f_1$  dominates  $f_3$  as well. If your manager asks you to define a priority order for these 3 faults during the ATPG, what priority order would you suggest? Provide the reason(s) for your answer. (5%)  $\rightarrow \{f_3 \rightarrow f_2 \rightarrow f_1\}$  The dominated faults are targeted first for ATPG. This may have a benefit to detecting the other easier faults that dominate it by the way.
  - (b) Consider a NOR gate realizing  $z=(a+b)'$ . What dominance relations you can derive among the 6 stuck-at faults  $\{a\text{-sa-0}, b\text{-sa-0}, z\text{-sa-1}\}$ ? (Hint: you can use any technique to derive the answer. One technique is to list the fault-free function and the faulty functions of the 6 stuck-at faults first. Then, the complete test set for each fault can be derived to find out the dominance relations among the 6 faults). (5%)  $\rightarrow z\text{-stuck-at-1 dominates } a\text{-sa-0, and } b\text{-sa-0}$
2. (15%) Consider the fault modeling of a PLA with the symbolic schematic shown below. Note that product line P2 has two branches, the one driving output line f1 is particularly called  $x$  (as shown in the right-hand-side of the figure below).
  - (a) Derive the fault-free Boolean function for output signal f1 of this PLA in the Sum-of-Product (SoP) form (5%).  $\rightarrow f1 = A'C + AB'$
  - (b) On the left-hand side of the figure, if there is a missing cross-point fault at the cross-point of (vertical) input line  $A'$  and (horizontal) product line P1, then what is the faulty Boolean expression for output signal f1, (Note: denote the name of this faulty signal as f1-faulty? (5%)  $\rightarrow f1\text{-faulty} = C + AB'$
  - (c) On the left-hand side of the figure, if there is a missing cross-point fault at the cross-point of (horizontal) product line P2 and (vertical) output line f1, then what stuck-at fault is this fault equivalent to on the circuit model on the right-hand-side? (Note: you have to specify the equivalent faulty signal name and the stuck-at value). (5%)  $\rightarrow x \text{ stuck-at-0}$



 3. (15%) Consider the technique of **critical-path tracing for fault simulation** based on the simulation results in response to an input vector  $(a,b,c,d)=(1,0,1,0)$  as shown below.
  - (a) Draw the circuit on your answer sheet and mark every *sensitive input* of each gate with a dot like in the lecture notes. (5%)  $\rightarrow$  As shown below.
  - (b) Derive the *critical lines*. Note that the critical-path tracing traverses the circuit from the outputs toward the inputs and stops whenever a stem is encountered. (5%)  $\rightarrow \{g, h, e, b1, d\}$
  - (c) Derive the *set of faults that can be detected* based on the information derived in (b). Follow the branch notations as shown in the figure. The faults on the primary inputs should also be considered. (5%)  $\rightarrow \{g/1, h/1, e/1, b1/1, d/1\}$



4. (10%) Consider a circuit realizing a Boolean function,  $f = (ab + c)$ .
- Derive the Boolean difference  $df/db$ . Express your answer as a Boolean expression. (Note: you can derive it by any technique.) (5%) →  $ac'$
  - Derive the only test pattern for  $b$  stuck-at 0. (5%) →  $(a, b, c) = (1, 1, 0)$
5. (20%) Consider the following questions related to the 5-valued D-algorithm for ATPG.
- When a signal is labeled as D or D', it is referred to have a fault effect. What does D' mean? → D' means '0/1', or it is required to have a value of 0 in the fault-free circuit, and a value of '1' in the faulty circuit.
  - During the execution of the D-algorithm for a specific stuck-at fault, an AND-gate's output, signal  $f$ , has an assignment of '0' and is included in the J-frontier. What can you say about the inputs of this AND gate at this moment? → Since  $f$  is in the J-Frontier, it is NOT JUSTIFIED YET. It follows that none of this AND gate's input signals is a controlling value of '0'.
  - There are two types of "decisions" in the D-algorithm. The first type is to choose one of the D-frontier for further fault effect propagation. What is the second type? → To choose a J-frontier signal to further justified toward the PIs.
  - During the execution of the D-algorithm, what condition will lead us to claim that the current fault under consideration is indeed "untestable"? (Note: the condition consists of two sub-conditions that hold at the same time. One is about the D-frontier and the other about the J-frontier). → The D-frontier is empty, while J-Frontier is not empty yet. All solution space has been exhausted yet, there is not valid test pattern.
6. (15%) Consider the following questions related to the PODEM algorithm for ATPG.
- PODEM performs a direct search on the primary inputs. Two routines are especially important to guide the search process, namely *objective()* and *backtrace()*. The routine *objective()* is to set up an objective as a signal-value pair. Describe the function of *backtrace()*. (5%) → According to an objective, find an all-x path to a PI, so that an assignment at that PI will be likely to contribute to the satisfaction of the current objective.
  - The SCOAP program, denoting SANDIA Controllability and Observability Analysis Program could provide useful guidance to speed up the PODEM search algorithm. Consider a two-input NAND-gate in the circuit under test,  $Z = (AB)'$ . If  $CC0(A)$ ,  $CC1(A)$ ,  $CC0(B)$ ,  $CC1(B)$  are 3, 6, 10, and 1, respectively. Compute  $CC0(Z)$ . (5%) →  $(6+1)+1 = 8$
  - Unlike the controllability measure calculation that is performed using a forward sweep of the circuit under test, the observability measure calculation is done by a backward (PO-to-PI) sweep. If the observability of  $Z$ , denoted as  $CO(Z)$ , has been calculated as 5, then what is

CO(A). (5%)  $\rightarrow (5+1)+1 = 7$

7. (15%) To detect a signal *f* *slow-to-rise transition delay fault*, a two-pattern test  $\langle v_1, v_2 \rangle$  is required.
- (a) State what requirement needs to be satisfied for vector  $v_1$  in the first time frame. (5%)  $\rightarrow v_1$  needs to cause signal *f* to logic '0' (or excite signal *a* stuck-at-1 fault)
  - (b) In the second time frame, the requirement of  $v_2$  is equivalent to the detection of a single-stuck-at fault. Name the stuck-at fault. (5%)  $\rightarrow v_2$  needs to be able to detect signal *f* stuck-at-0 fault in the 2nd time frame.
  - (c) Suppose that  $v_1 = \{y_1, y_2, y_3\} = (1, 1, 0)$  and  $v_2 = \{y_1, y_2, y_3\} = (1, 1, 0)$  are two vectors satisfying all the above two requirements. Signals  $\{y_1, y_2, y_3\}$  are PPI signals in the scan chain in the order of ( $SI \rightarrow y_3 \rightarrow y_2 \rightarrow y_1 \rightarrow SO$ ). Can we apply  $\langle v_1, v_2 \rangle$  under the *Launch-off-Shifting* (LOS) scheme? Why? (5%)  $\rightarrow$  NO,  $v_1$  cannot become  $v_2$  after one cycle of scan shifting operation.